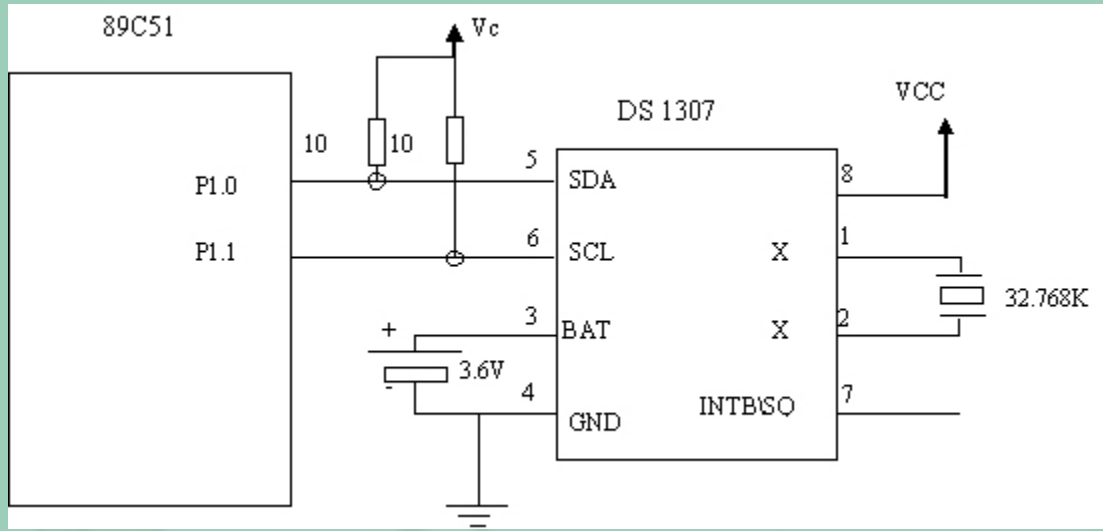


- ❖ Knows about the interfacing with keyboards
- ❖ Knows about the interfacing with LED's.
- ❖ Knows about the interfacing with LCD's
- ❖ Knows about the interfacing with ADC, DAC etc.
- ❖ Knows about external program and data memory interface.




RTC Interface




- DS 1307 is a real time clock chip
- Maintains real time clock once powered up Year, Month, Day, Time in hours, Minutes and seconds can be written into or read out serially
- Has 56 bytes of data space to save or retrieve data of importance like settings
- Consumes very low power 2 or 3 μw @ 32.768KHz with a backup battery of 2.5 to 3.6V
- Has SDA, SCL pins to send data and clock respectively
- SDA, SCL are directly interfaced to I/O pins of 89C51

Keyboard Interface-1

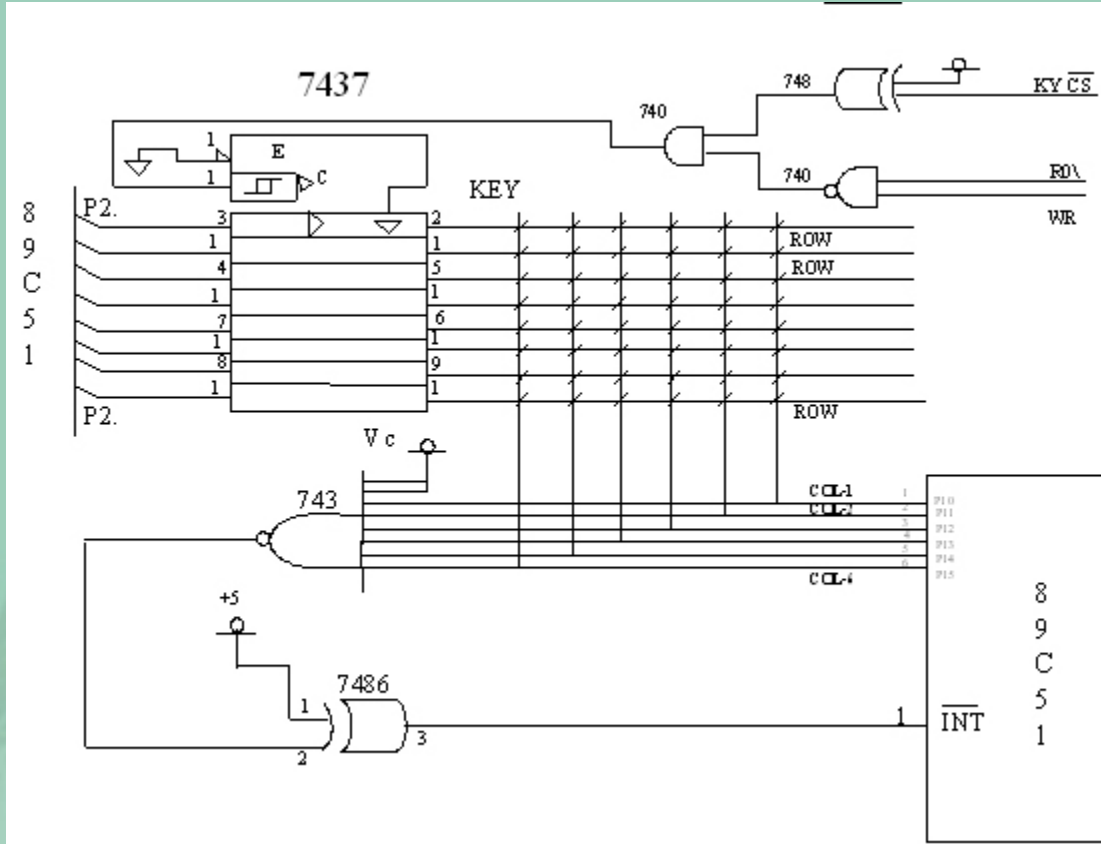

- Outputs 8 bit row code (0FEH, 0FDH etc..) on port0
- Interrupts micro-controller when a key is pressed
- Interrupt software to find which column and key is pressed


Keyboard Interface -2

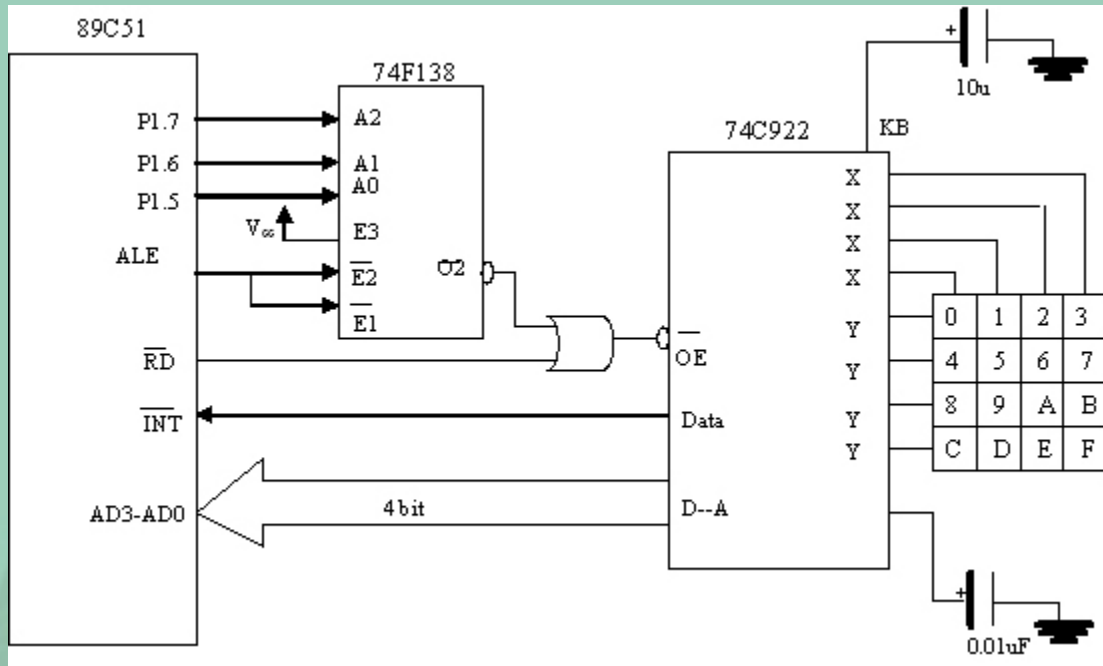

Keyboard Interface-2


- 74C922 is a 16 key encoder that performs keypad scanning and de-bouncing
- When key is pressed it outputs a 4 bit code
- When interfaced to micro-controller, it reads the code through its port pins
- Has key De-bouncing and key mask features
- It has a data available output that interrupts the micro-controller
- Interrupt software to find the key pressed

Keyboard Interface-3

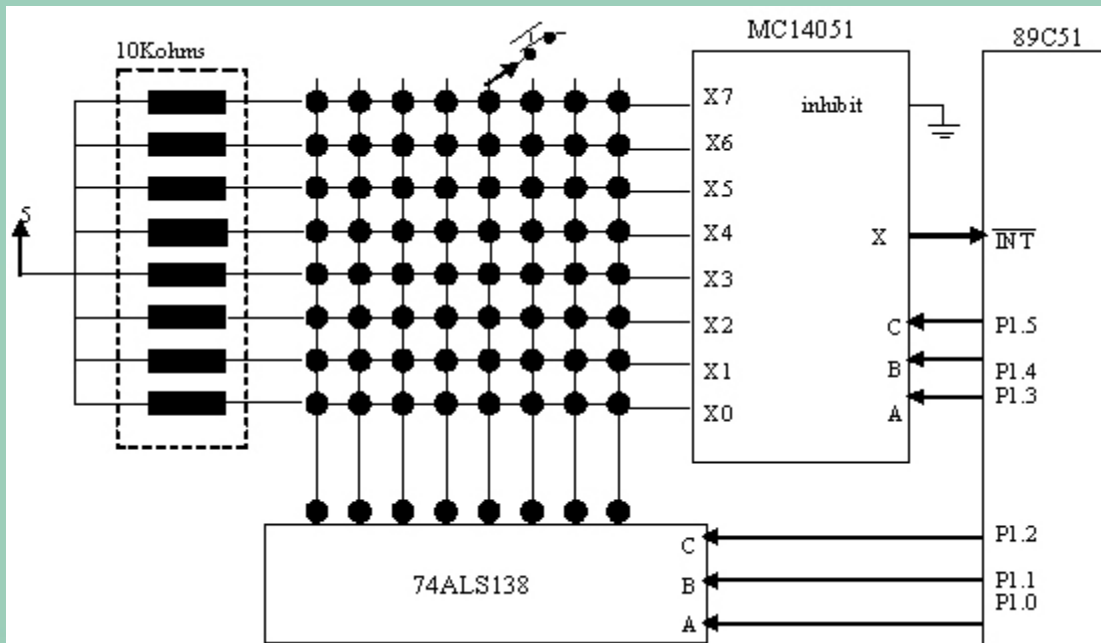


- The circuit interfaces 64 keys
- It consists of 14051 a 8:1 multiplexer and 74138 a 3:8 decoder
- When a key is pressed 89C51 is interrupted
- The 3 bit input of multiplexer and 3 bit input of the decoder gives the key code
- which is read in the interrupt routine

Serial ADC Interface

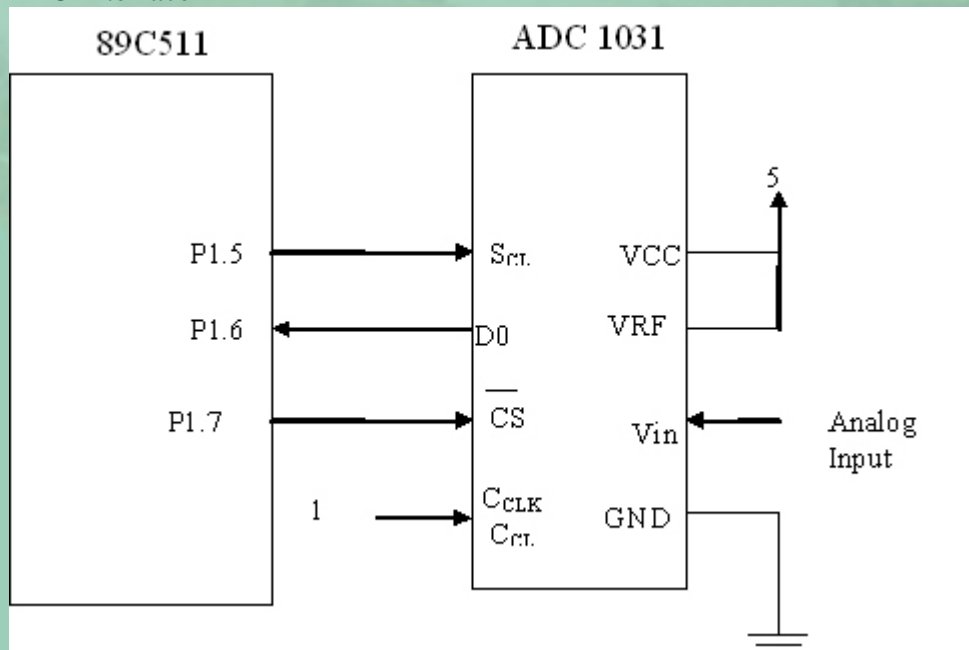


Battery Backup

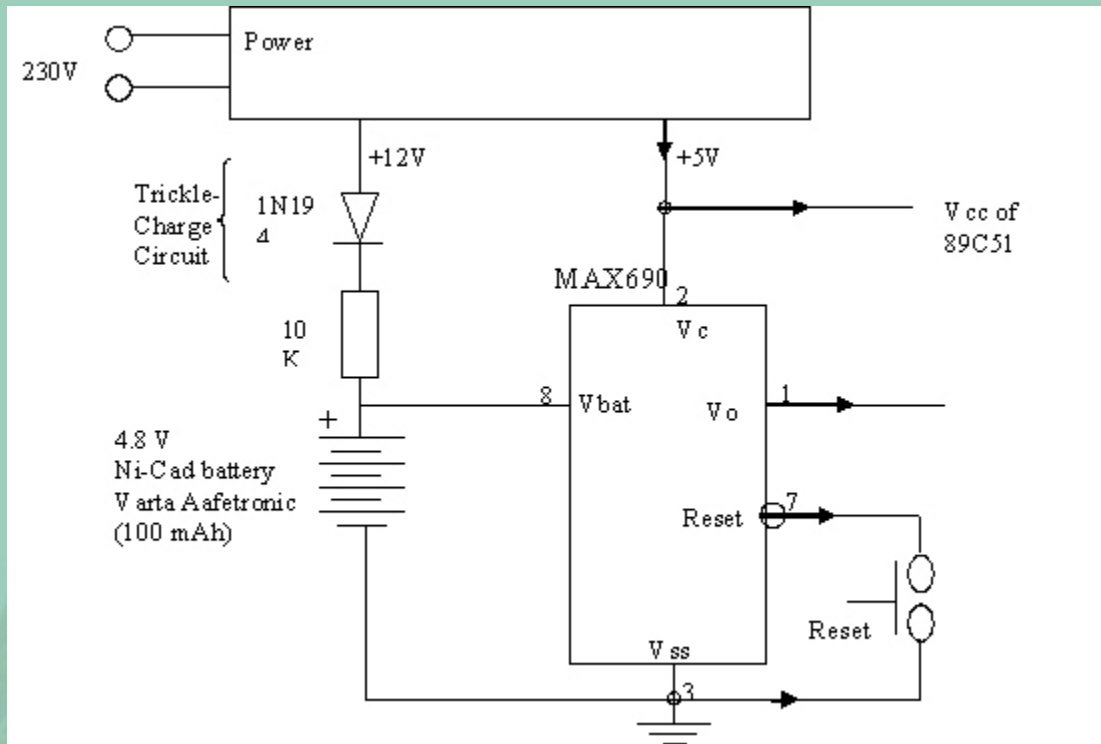

- Max 690 is a battery switchover/reset generator chip
- It provides a voltage threshold mechanism for bringing the chip out of reset at startup and for returning it to reset at power down
- The reset out is connected to the reset pin of 89C51 through an inverter
- V_OUT is connected to the V_{CC} of any memory chip which requires battery backup

Serial Interface

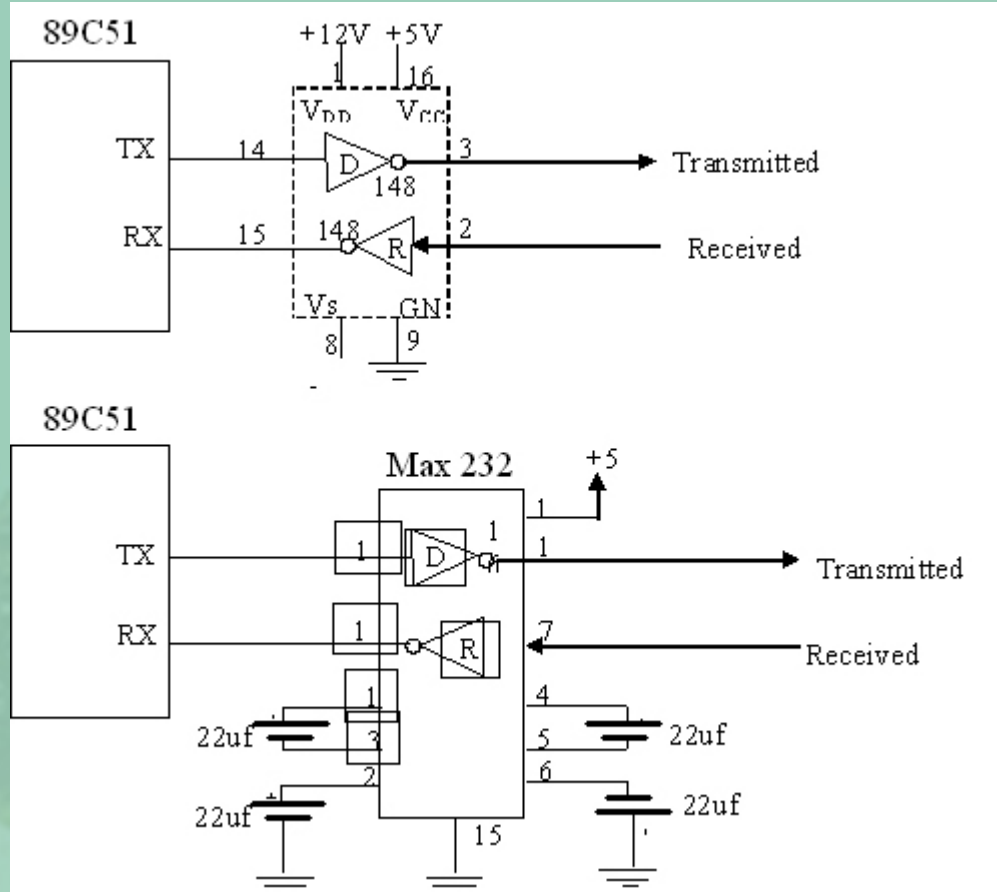


- RS 232 interface can be realised with 1488 (transmitter) and 1489 (receiver) level translator ICs
- These ICs require $\pm 12V$ supplies
- Max 232 IC require only 5V and four external capacitors

LCD Interface

- LCD module LM015 displays one line of 16 characters.
- LM015 is initialized with some command words through its control register
- The data to be displayed is written into its data register in ASCII format
- RS pin distinguishes the control and data registers when E is logic high

LED Interface-1

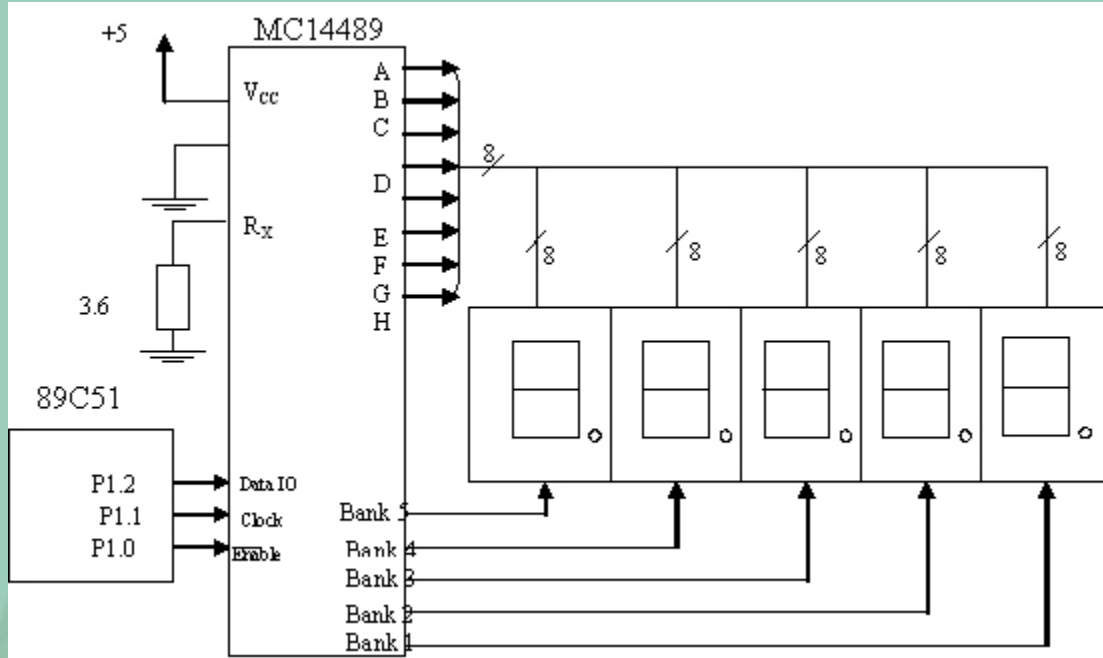

- MC14489 is a multi character LED driver
- Without additional ICs 89C51 can be interfaced to drive five 7 Segment LED displays.
- 24 bit data is serially transmitted to the driver by the 89C51 to display five digits with decimal point option
- MC14489s can be cascaded for more number of displays
- The brightness is controlled by the external resistor 3.6K

1. In 8051 an external interrupt 1 vector address is of _____ and causes of interrupt if _____.
 - a) 000BH, a high to low transition on pin INT1
 - b) 001BH, a low to high transition on pin INT1
 - c) 0013H, a high to low transition on pin INT1
 - d) 0023H, a low to high transition on pin INT1

2. Serial port vector address is of _____. And causes an interrupt when _____.
 - a) 0013H, either TI or RI flag is set
 - b) 0023H, either TI or RI flag is reset
 - c) 0013H, either TI or RI flag is reset
 - d) 0023H, either TI or RI flag is set

3. In serial communication modes, mode 1 the Baud rate =
 - a) $BR=2^{SMOD}/32 * (\text{Timer 0 over flow rate})$
 - b) $BR=2^{SMOD}/16 * (\text{Timer 1 over flow rate})$
 - c) $BR=2^{SMOD}/16 * (\text{Timer 0 over flow rate})$
 - d) $BR=2^{SMOD}/32 * (\text{Timer 1 over flow rate})$

4. In modes 2 and 3, if _____ bit of SCON bit is set will causes enable multiprocessor communication and is of _____ bit address.
 - a) SM1, 9EH
 - b) TB8, 9CH
 - c) SM2, 9DH
 - d) SM0, 9FH

5. Interfacing LCD with 89C51 _____ data lines are used along with the _____ signals.
 - a) 6, RS, RW
 - b) 5, RW, EN
 - c) 8, RS, EN, RW
 - d) 9, RS, EN, RW

6. Resolution of ADC is defined as
 - a) $1/(2^N - 1)$
 - b) $2^N - 1$
 - c) $1/(2^N - 1)$
 - d) $2^N - 1$

7. In microcontroller and LCD interface which line will instruct the LCD that microcontroller is sending data?
 - a) DB0
 - b) RW
 - c) EN
 - d) RS

8. Which bit of TMOD will exactly configure timer / counter as a timer or counter.
 - i) TMOD.6 of C/T for timer 1
 - ii) TMOD.6 of C/T for timer 0
 - iii) TMOD.2 of C/T for timer 0
 - iv) TMOD.2 of C/T for timer 1
 - a) i, ii
 - b) ii, iv
 - c) i, iii
 - d) iii, iv

Key:

7.1 C

7.2 D

7.3 D

7.4 C

7.5 C

7.6 C

7.7 C

7.8 C

